

NCERT Physics 12.7 Q21

EE23BTECH11009 - AROSHISH PRADHAN*

Question: Obtain the resonant frequency and Q-factor of a series LCR circuit with $L = 3.0 \text{ H}$, $C = 27 \mu\text{F}$, and $R = 7.4 \Omega$. It is desired to improve the sharpness of the resonance of the circuit by reducing its 'full width at half maximum' by a factor of 2. Suggest a suitable way.

Solution: Given parameters are:

Parameter	Value
L	3.0 H
C	$27 \mu\text{F}$
R	7.4Ω

TABLE I: Given Parameters

Resonance Frequency (ω_0) is given by:

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

Substituting values of L and C gives:

$$\begin{aligned} \omega_0 &= \frac{1}{\sqrt{3 \cdot 27 \times 10^{-6}}} \\ &= \frac{10^3}{9} \text{ s}^{-1} \\ &= 111.12 \text{ s}^{-1} \end{aligned} \quad (1)$$

Quality Factor (Q) is given by:

$$Q = \frac{1}{R} \cdot \sqrt{\frac{L}{C}}$$

Substituting values of R, L and C gives:

$$\begin{aligned} Q &= \frac{1}{7.4} \cdot \sqrt{\frac{3}{27 \times 10^{-6}}} \\ &= \frac{10^3}{22.2} \\ &\approx 45 \end{aligned} \quad (4)$$

To reduce the full width at half maximum by a factor of 2, the quality factor needs to be doubled. One

way of doing this is to reduce the resistance by a factor of 2.

$$R' = \frac{R}{2} \quad (7)$$

$$= \frac{7.4}{2} \Omega \quad (8)$$

$$= 3.7 \Omega \quad (9)$$

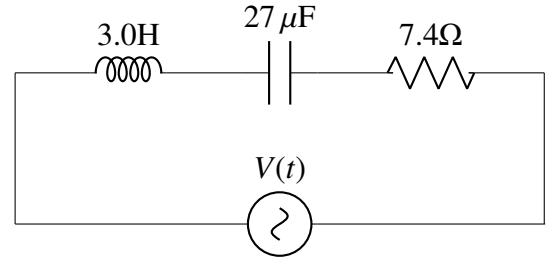


Fig. 1: LCR Circuit

Frequency Response of the Circuit

This is a series LCR circuit, with the elements in series with the voltage source. Applying Kirchhoff's Voltage Law (KVL), we get:

$$V_R + V_L + V_C = V(t) \quad (10)$$

- (2) where V_R , V_L and V_C are the voltages across R, L and C respectively and $V(t)$ is the time-varying voltage source.
- (3)

Substituting,

$$V_R = R \cdot I(t) \quad (11)$$

$$V_L = L \frac{dI(t)}{dt} \quad (12)$$

$$V_C = V(0) + \frac{1}{C} \int_0^t I(\tau) d\tau \quad (13)$$

into equation (10), we get:

$$R \cdot I(t) + L \frac{dI(t)}{dt} + V(0) + \frac{1}{C} \int_0^t I(\tau) d\tau = V(t) \quad (14)$$

The response of the circuit can be analysed at the transient and steady state by using the Laplace

Transform.

The Laplace Transform $F(s)$ of a function $f(t)$, defined for all real $t > 0$, is defined by

$$\mathcal{L}\{f\} = F(s) = \int_0^{\infty} f(t)e^{-st} dt \quad (15)$$

where s is a complex frequency domain parameter, i.e. $s = \alpha + i\omega$ ($\alpha, \omega \in \mathbf{R}$)

Applying the Laplace Transform to equation (14), we get

$$V(s) = I(s) \left(R + Ls + \frac{1}{sC} \right) \quad (16)$$

$$\Rightarrow I(s) = \frac{V(s)}{\left(R + Ls + \frac{1}{sC} \right)} \quad (17)$$

The term $\frac{I(s)}{V(s)}$ is called the Laplace Admittance $Y(s)$.

$$\Rightarrow Y(s) = \frac{I(s)}{V(s)} = \frac{s}{L \left(s^2 + \frac{R}{L}s + \frac{1}{LC} \right)} \quad (18)$$

We now define two terms: Neper Frequency (α) and Angular Resonance Frequency (ω_0).

Neper Frequency or Attenuation is a measure of how fast the transient response of a circuit will die out after the source has been removed.

For a series LCR circuit,

$$\alpha = \frac{R}{2L} \quad (19)$$

$$\omega_0 = \frac{1}{\sqrt{LC}} \quad (20)$$

Equation (18) can then be written as

$$Y(s) = \frac{s}{L(s^2 + 2\alpha s + \omega_0^2)} \quad (21)$$

The poles of $Y(s)$ are the values of s for which $Y(s) \rightarrow \infty$, i.e.

$$s^2 + 2\alpha s + \omega_0^2 = 0 \quad (22)$$

$$\Rightarrow s = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} \quad (23)$$

which are identical to the roots of the characteristic equation of equation (14).

For the given values of R , L and C we get

$$\alpha = \frac{R}{2L} = 1.234 s^{-1} \quad (24)$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = 111.12 s^{-1} \quad (25)$$

As $\omega_0 > \alpha$, values of s are imaginary. The frequency response of this circuit is therefore underdamped. The solution for $I(t)$ is given by inverse Laplace transform of $I(s)$:

$$I(t) = \frac{1}{L} \int_0^t V(t-\tau) e^{-\alpha\tau} \left[\cosh(\omega_d\tau) - \frac{\alpha}{\omega_d} \sinh(\omega_d\tau) \right] d\tau \quad (26)$$

where $\omega_d = \sqrt{\omega_0^2 - \alpha^2} = 111.11 s^{-1}$ is the damped frequency of oscillation.

The integral yields the transient response:

$$I(t) = e^{-\alpha t} [B_1 \cos(\omega_d t) + B_2 \sin(\omega_d t)] \quad (27)$$

where B_1 and B_2 are constants. Substituting $\alpha = 1.234 s^{-1}$ and $\omega_d = 111.11 s^{-1}$ we get

$$I(t) = e^{-1.234t} [B_1 \cos(111.11t) + B_2 \sin(111.11t)] \quad (28)$$

where t is in seconds. Constants B_1 and B_2 can be determined by the initial conditions of the given circuit.

The steady-state response of the circuit will depend on the nature of input $V(t)$. The transient and steady-state responses of the circuit can be added to give the net equation of $I(t)$.

The current $I(t)$ will fluctuate in a sinusoidal manner and decay over time. The frequency response of the circuit is underdamped response.