

NCERT Math 11.9.2 Q8

EE23BTECH11009 - AROSHISH PRADHAN*

Question: An input voltage in the form of a square wave of frequency 1 kHz is given to a circuit, which results in the output shown schematically below. Which one of the following options is the CORRECT representation of the circuit?


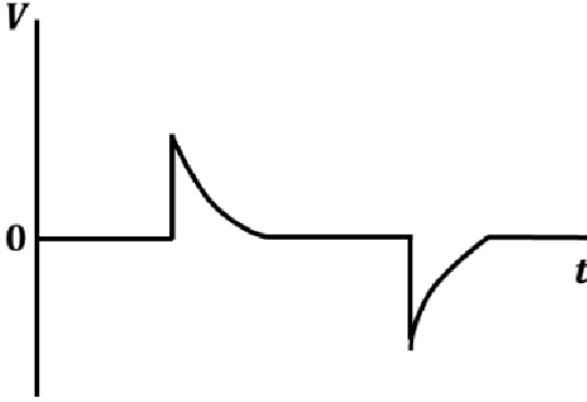


Fig. 1

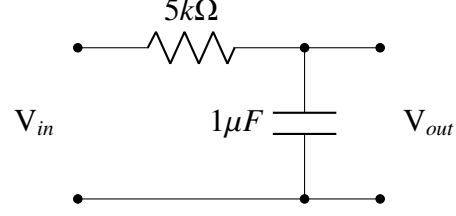

Solution:

Symbol	Value	Description
$V_{in}(t)$		Input Voltage
$\mathcal{V}_{in}(f)$		Fourier Transform of $V_{in}(t)$
$V_{out}(t)$		Output Voltage
$\mathcal{V}_{out}(f)$		Fourier Transform of $V_{out}(t)$
f	1000Hz	Input Wave Frequency
T	$\frac{1}{f} = 10^{-3}\text{s}$	Input Wave Time Period
R	(a) $0.5\text{k}\Omega$ (b) $5\text{k}\Omega$	Resistance
C	(a) $0.1\mu\text{F}$ (b) $1\mu\text{F}$	Capacitance
τ	RC	Time Constant
Z	$R + \frac{1}{sC}$	Impedance
$H(f)$	$\frac{V_{out}}{V_{in}}$	General Transfer Function
$H_R(f)$	$\frac{V_{R,out}}{V_{in}}$	Transfer Function for Resistor
$H_C(f)$	$\frac{V_{C,out}}{V_{in}}$	Transfer Function for Capacitor

TABLE I: Given Parameters

Input waveform is a square wave (Fig. 2), so we take its Fourier Transform as shown in Fig. 4

$$V_{in}(t) = 2 \left(2 \left[\frac{\left(t - \frac{T}{4}\right)}{T} \right] - \left[\frac{2\left(t - \frac{T}{4}\right)}{T} \right] \right) + 1 \quad (1)$$

Fourier Series Coefficient:

$$c_k = \frac{1}{T} \int_T V_{in}(t) e^{-jk2\pi ft} dt \quad (2)$$


As square wave is even, $\sin(k2\pi ft)$ terms become zero. Cosine coefficients are:

$$a_n = \frac{2}{T} \int_T V_{in}(t) \cos\left(\frac{2\pi nt}{T}\right) dt \quad (3)$$

$$= \frac{4}{n\pi} \sin\left(\frac{n\pi}{2}\right) \cos(n\pi) \quad (4)$$

Fourier Series of $V_{in}(t)$, visualized in Fig. 2:

$$V_{in}(t) = \sum_{n=1}^{\infty} a_n \cos\left(\frac{2\pi nt}{T}\right) \quad (5)$$

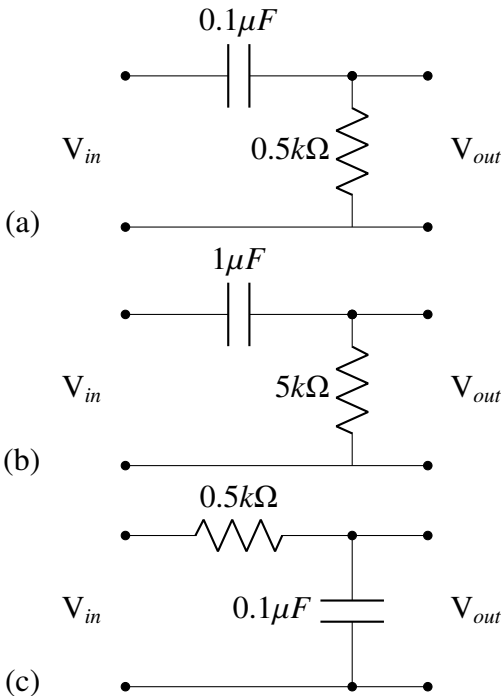

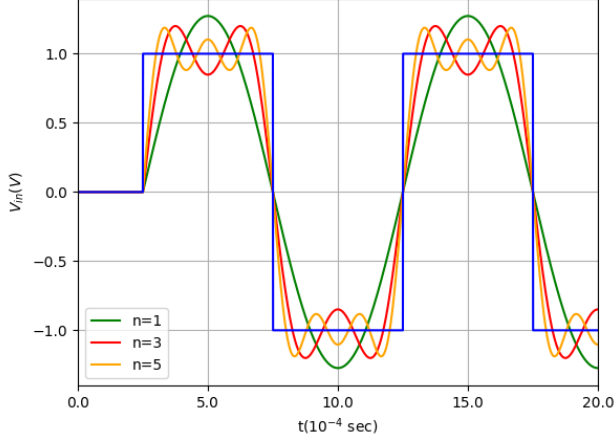


Fig. 2: Input Square Waveform ($V_{in}(t)$)

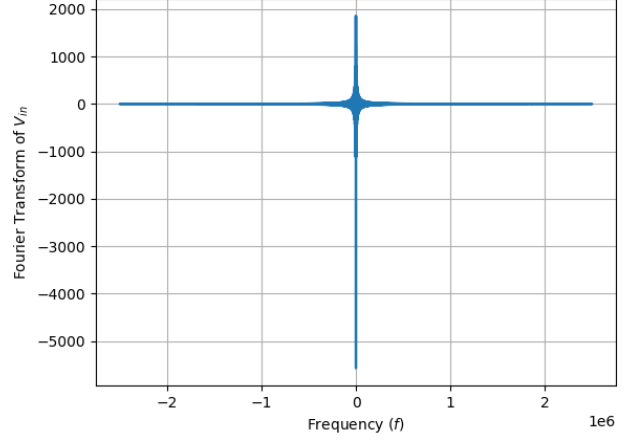


Fig. 4: $\mathcal{V}_{in}(f)$ (Fourier Transform of $V_{in}(t)$)

Taking Fourier Transform of $V_{in}(t)$, plotted in Fig. 4:

$$V_{in}(t) \xleftrightarrow{\mathcal{F}} \mathcal{V}_{in}(f) \quad (6)$$

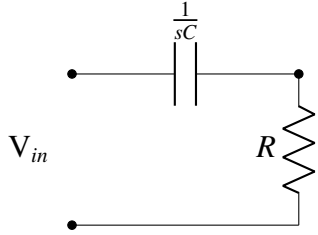


Fig. 3: Series RC Circuit in s-domain

$$s = j2\pi f \quad (7)$$

$$\Rightarrow Z = R + \frac{1}{sC} \quad (8)$$

$$= R + \frac{1}{j2\pi fC} \quad (9)$$

$$H(f) = \frac{V_{out}}{V_{in}} \quad (10)$$

Across R,

$$H_R(f) = \frac{R}{R + \frac{1}{j2\pi fC}} \quad (11)$$

$$\Rightarrow \mathcal{V}_{out}(f) = H_R(f)\mathcal{V}_{in}(f) \quad (12)$$

Across C,

$$H_C(f) = \frac{\frac{1}{j2\pi fC}}{R + \frac{1}{j2\pi fC}} \quad (13)$$

$$\Rightarrow \mathcal{V}_{out}(f) = H_C(f)\mathcal{V}_{in}(f) \quad (14)$$

$$\mathcal{V}_{out}(f) \xleftrightarrow{\mathcal{F}} V_{out}(t) \quad (15)$$

$\mathcal{V}_{in}(f)$ was input into all four circuits and Inverse Fourier Transform was taken of the response. All responses are plotted below:

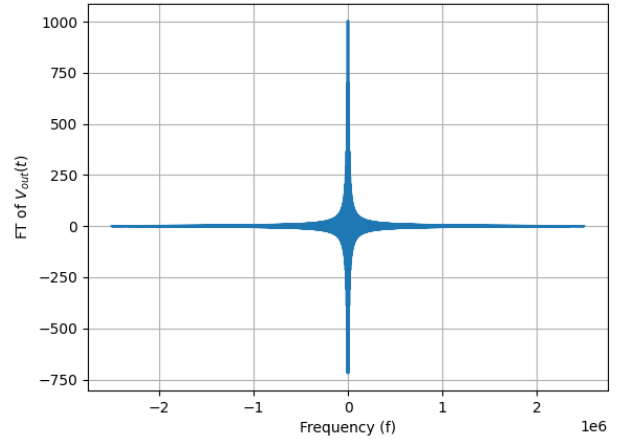


Fig. 5: Opt A: Fourier Transform of $V_{out}(t)$

As Fig. 6 resembles question Fig. 1, option (a) is the correct answer.

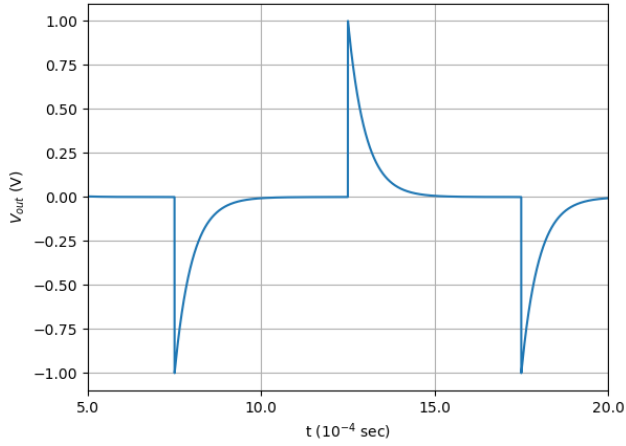


Fig. 6: Opt A: Response

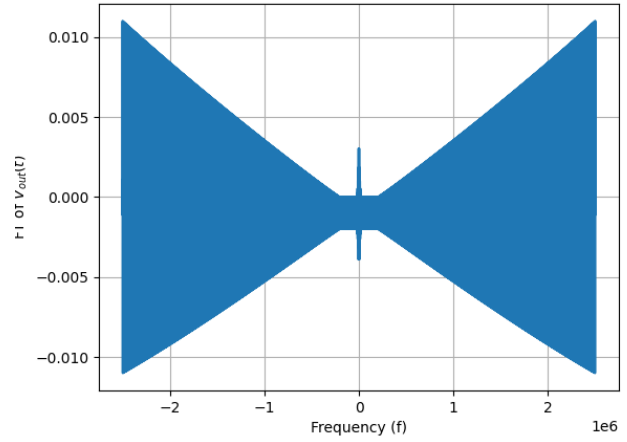
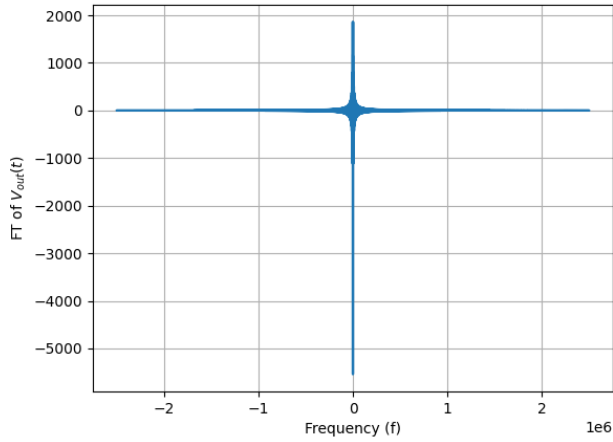
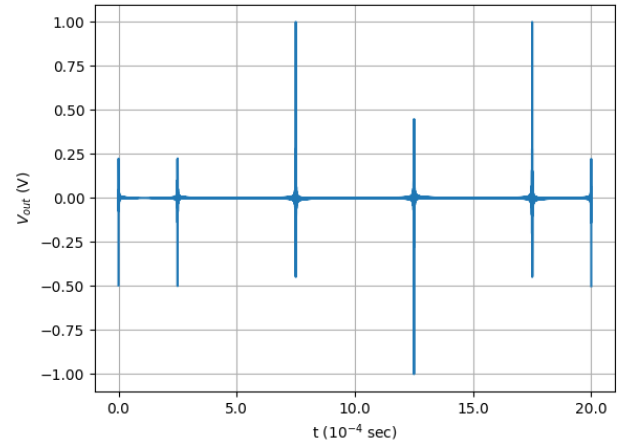
Fig. 9: Opt C: Fourier Transform of $V_{out}(t)$ Fig. 7: Opt B: Fourier Transform of $V_{out}(t)$ 

Fig. 10: Opt C: Response

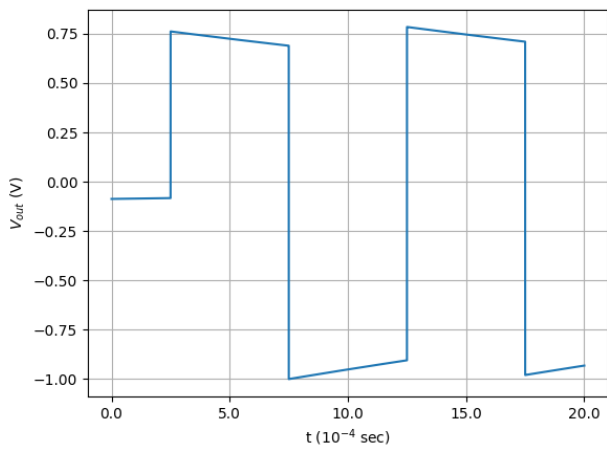
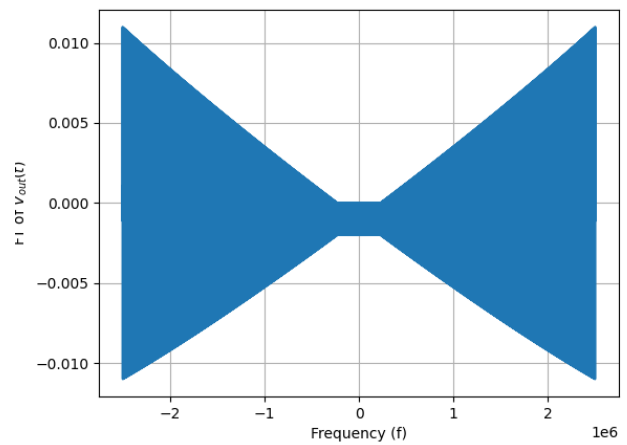


Fig. 8: Opt B: Response

Fig. 11: Opt D: Fourier Transform of $V_{out}(t)$

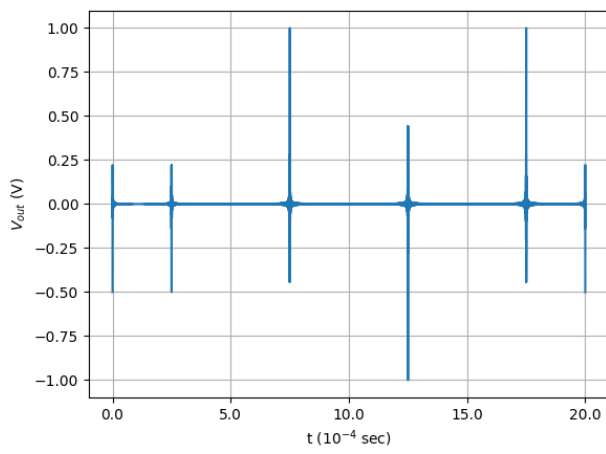


Fig. 12: Opt D: Response