

NCERT Math 11.9.2 Q8

EE23BTECH11009 - AROSHISH PRADHAN*

Question: An input voltage in the form of a square wave of frequency 1 kHz is given to a circuit, which results in the output shown schematically below. Which one of the following options is the CORRECT representation of the circuit?


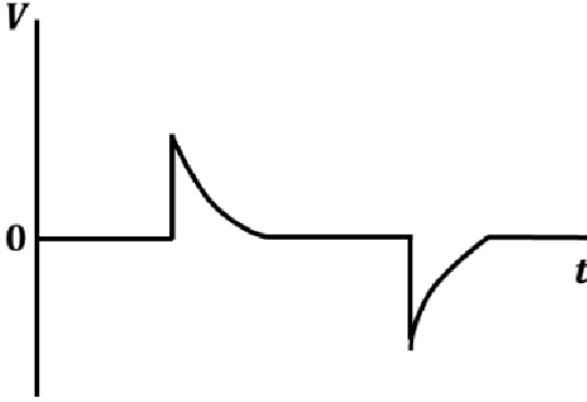


Fig. 1

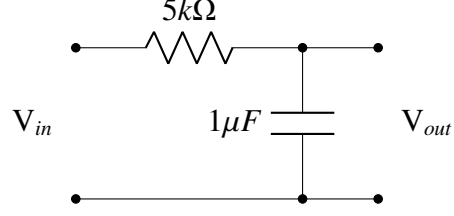

(d)

Solution:

Symbol	Value	Description
$V_{in}(t)$		Input Voltage
$\mathcal{V}_{in}(j\omega)$		Fourier Transform of $V_{in}(t)$
$V_{out}(t)$		Output Voltage
$\mathcal{V}_{out}(j\omega)$		Fourier Transform of $V_{out}(t)$
$I(t)$		Current
$\mathcal{I}(j\omega)$		Fourier Transform of $I(t)$
f	$\frac{\omega}{2\pi} = 1000\text{Hz}$	Input Wave Frequency
T	$\frac{2\pi}{\omega} = 10^{-3}\text{s}$	Input Wave Time Period
R	(a) $0.5\text{k}\Omega$ (b) $5\text{k}\Omega$	Resistance
C	(a) $0.1\mu\text{F}$ (b) $1\mu\text{F}$	Capacitance
τ	RC	Time Constant
Z	$R + \frac{1}{j\omega C}$	Impedance
$H(j\omega)$	$\frac{V_{out}}{V_{in}}$	General Transfer Function
$H_R(j\omega)$	$\frac{V_{R,out}}{V_{in}}$	Transfer Function for Resistor
$H_C(j\omega)$	$\frac{V_{C,out}}{V_{in}}$	Transfer Function for Capacitor

TABLE I: Given Parameters

Input waveform is a square wave (Fig. 2), so we take its Fourier Transform as shown in Fig. 4

$$V_{in}(t) = 2 \left(2 \left[\frac{\left(t - \frac{T}{4}\right)}{T} \right] - \left[\frac{2\left(t - \frac{T}{4}\right)}{T} \right] \right) + 1 \quad (1)$$


Fourier Series Coefficient:

$$c_k = \frac{1}{T} \int_T V_{in}(t) e^{-jk2\pi ft} dt \quad (2)$$

As square wave is even, $\sin(k2\pi ft)$ terms become zero. Cosine coefficients are:

$$a_n = \frac{2}{T} \int_T V_{in}(t) \cos\left(\frac{2\pi nt}{T}\right) dt \quad (3)$$

$$= \frac{4}{n\pi} \sin\left(\frac{n\pi}{2}\right) \cos(n\pi) \quad (4)$$

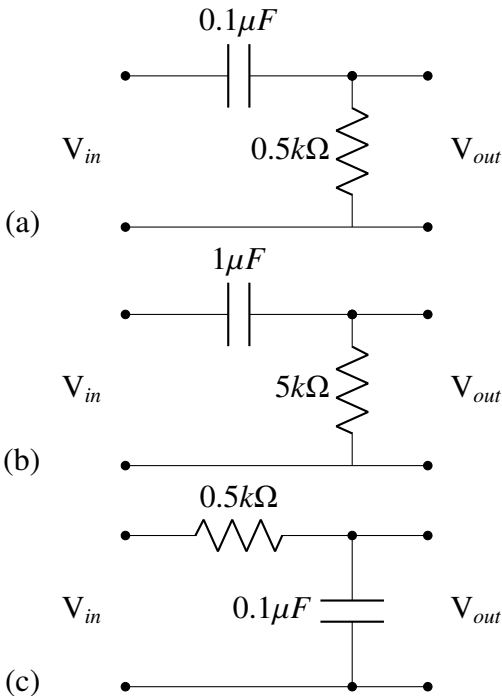

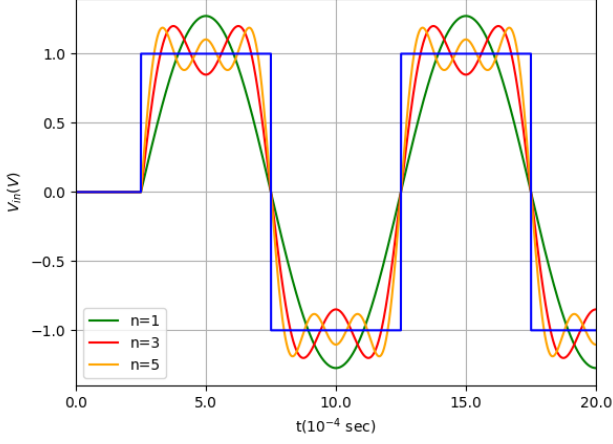


Fig. 2: Input Square Waveform ($V_{in}(t)$)

Fourier Series of $V_{in}(t)$, visualized in Fig. 2:

$$V_{in}(t) = \sum_{n=1}^{\infty} a_n \cos\left(\frac{2\pi n t}{T}\right) \quad (5)$$

Taking Fourier Transform of $V_{in}(t)$, plotted in Fig. 4:

$$V_{in}(t) \xleftrightarrow{\mathcal{F}} \mathcal{V}_{in}(j\omega) \quad (6)$$

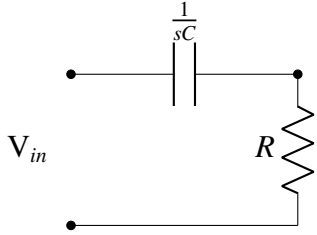


Fig. 3: Series RC Circuit in s-domain

$$s = j\omega \quad (7)$$

$$\Rightarrow Z = R + \frac{1}{sC} \quad (8)$$

$$= R + \frac{1}{j\omega C} \quad (9)$$

Applying KVL:

$$\mathcal{V}_{in}(j\omega) = I(j\omega) \left(R + \frac{1}{j\omega C} \right) \quad (10)$$

$$\Rightarrow I(j\omega) = \frac{\mathcal{V}_{in}(j\omega)}{\left(R + \frac{1}{j\omega C} \right)} \quad (11)$$

\therefore output across R:

$$= RI(j\omega) \quad (12)$$

$$= \frac{R}{\left(R + \frac{1}{j\omega C} \right)} \mathcal{V}_{in}(j\omega) \quad (13)$$

and output across C:

$$= \frac{1}{j\omega C} I(j\omega) \quad (14)$$

$$= \frac{\frac{1}{j\omega C}}{\left(R + \frac{1}{j\omega C} \right)} \mathcal{V}_{in}(j\omega) \quad (15)$$

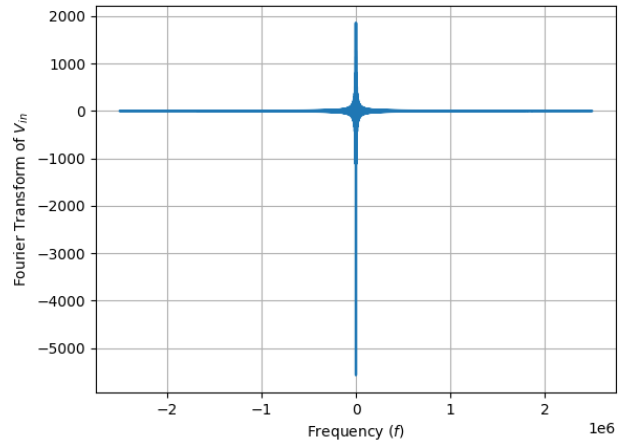


Fig. 4: $\mathcal{V}_{in}(j\omega)$ (Fourier Transform of $V_{in}(t)$)

$\mathcal{V}_{in}(j\omega)$ was input into all four circuits and Inverse Fourier Transform was taken of the response. All responses are plotted below:

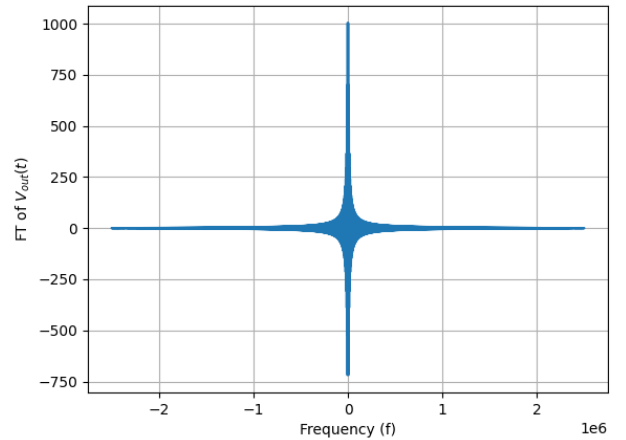


Fig. 5: Opt A: Fourier Transform of $V_{out}(t)$

As Fig. 6 resembles question Fig. 1, option (a) is the correct answer.

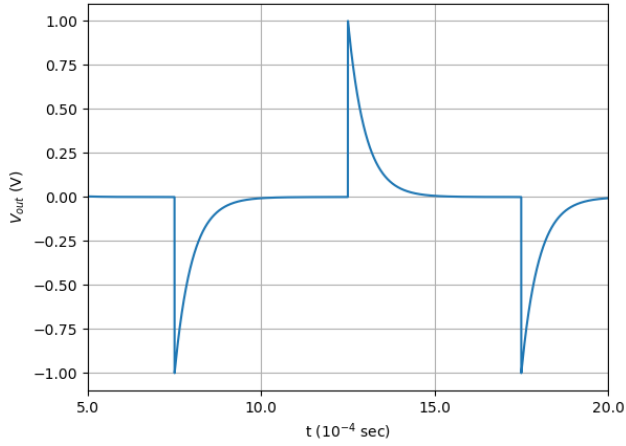


Fig. 6: Opt A: Response

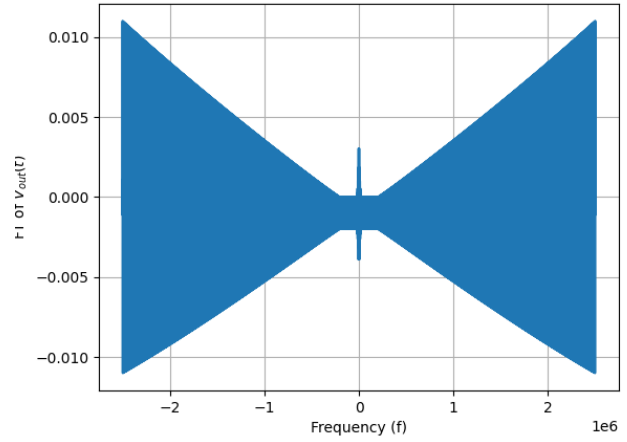
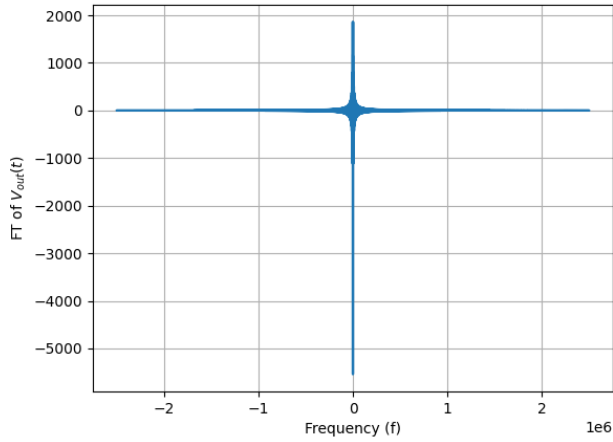
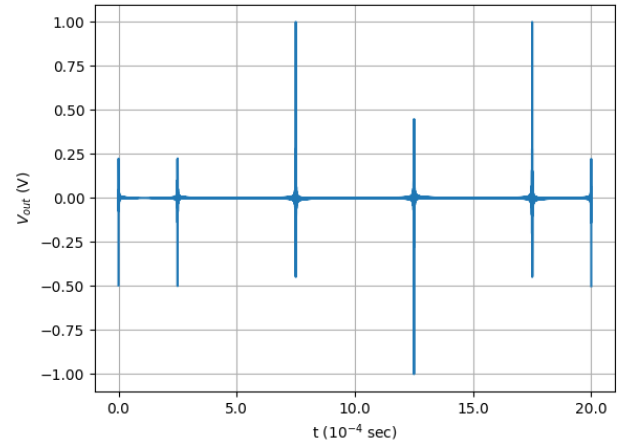
Fig. 9: Opt C: Fourier Transform of $V_{out}(t)$ Fig. 7: Opt B: Fourier Transform of $V_{out}(t)$ 

Fig. 10: Opt C: Response

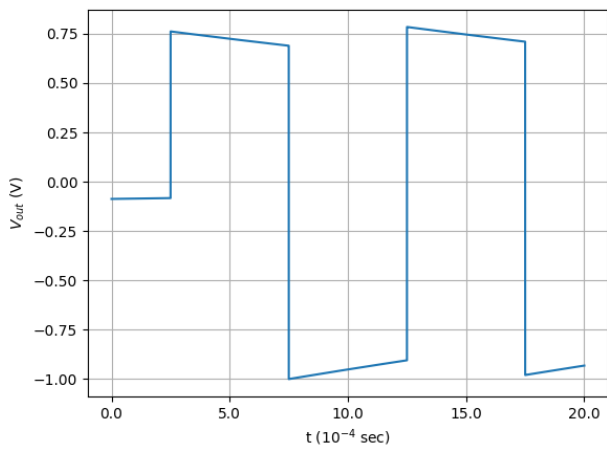
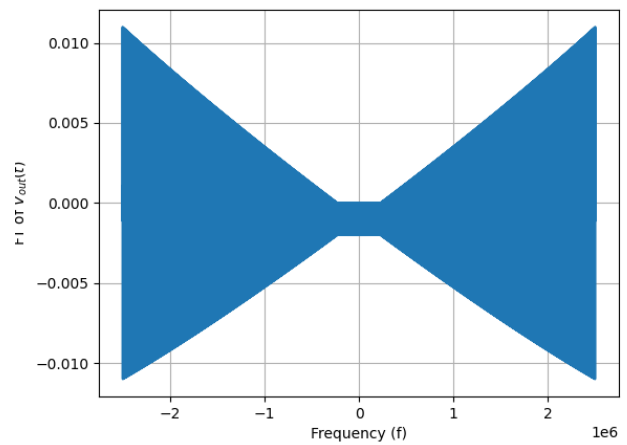


Fig. 8: Opt B: Response

Fig. 11: Opt D: Fourier Transform of $V_{out}(t)$

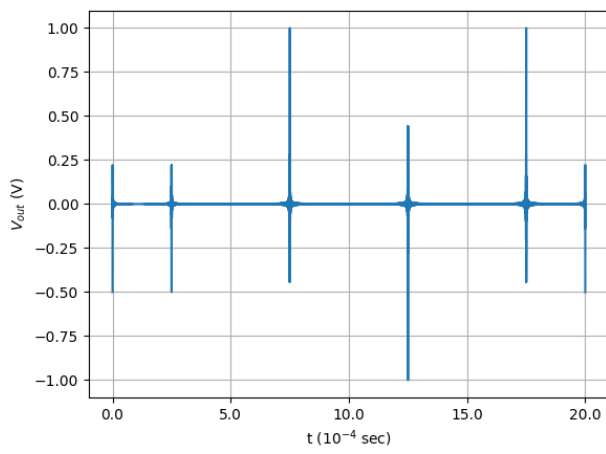


Fig. 12: Opt D: Response