

# GATE 2023 PH Q37

EE23BTECH11009 - AROSHISH PRADHAN\*

**Question:** An input voltage in the form of a square wave of frequency  $1\text{ kHz}$  is given to a circuit, which results in the output shown schematically below. Which one of the following options is the CORRECT representation of the circuit?


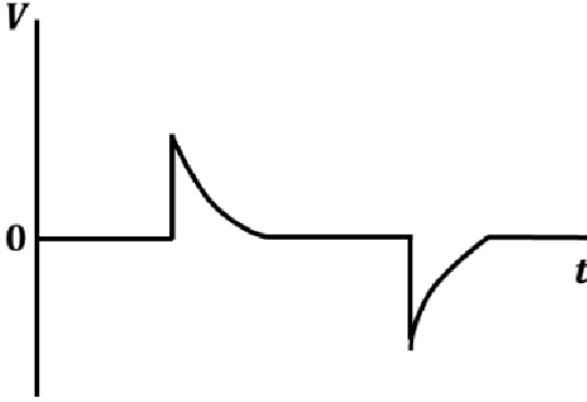


Fig. 1

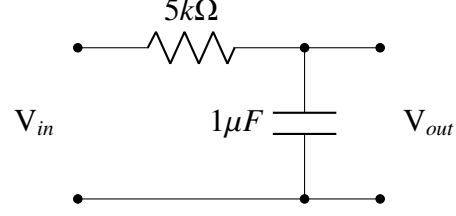

**Solution:**

Symbol	Value	Description
$V_{in}(t)$		Input Voltage
$\mathcal{V}_{in}(j\omega)$		Fourier Transform of $V_{in}(t)$
$V_{out}(t)$		Output Voltage
$\mathcal{V}_{out}(j\omega)$		Fourier Transform of $V_{out}(t)$
$f$	$\frac{\omega}{2\pi} = 1000\text{Hz}$	Input Wave Frequency
$T$	$\frac{2\pi}{\omega} = 10^{-3}\text{s}$	Input Wave Time Period
$R$	(a) $0.5\text{k}\Omega$ (b) $5\text{k}\Omega$	Resistance
$C$	(a) $0.1\mu\text{F}$ (b) $1\mu\text{F}$	Capacitance
$\tau$	$RC$	Time Constant
$Z$	$R + \frac{1}{j\omega C}$	Impedance
$H(j\omega)$	$\frac{V_{out}}{V_{in}}$	General Transfer Function
$H_R(j\omega)$	$\frac{V_{R,out}}{V_{in}}$	Transfer Function for Resistor
$H_C(j\omega)$	$\frac{V_{C,out}}{V_{in}}$	Transfer Function for Capacitor

TABLE I: Given Parameters

Input waveform is a square wave (Fig. 2), so we take its Fourier Transform

$$V_{in}(t) = 2 \left( 2 \left[ \frac{\left(t - \frac{T}{4}\right)}{T} \right] - \left[ \frac{2\left(t - \frac{T}{4}\right)}{T} \right] \right) + 1 \quad (1)$$

Fourier Series Coefficient:

$$c_k = \frac{1}{T} \int_T V_{in}(t) e^{-jk\omega t} dt \quad (2)$$


As square wave is even,  $\sin(k\omega t)$  terms become zero. Cosine coefficients are:

$$a_n = \frac{2}{T} \int_T V_{in}(t) \cos\left(\frac{2\pi n t}{T}\right) dt \quad (3)$$

$$= \frac{4}{n\pi} \sin\left(\frac{n\pi}{2}\right) \cos(n\pi) \quad (4)$$

Fourier Series of  $V_{in}(t)$ , visualized in Fig. 2:

$$V_{in}(t) = \sum_{n=1}^{\infty} a_n \cos\left(\frac{2\pi n t}{T}\right) \quad (5)$$

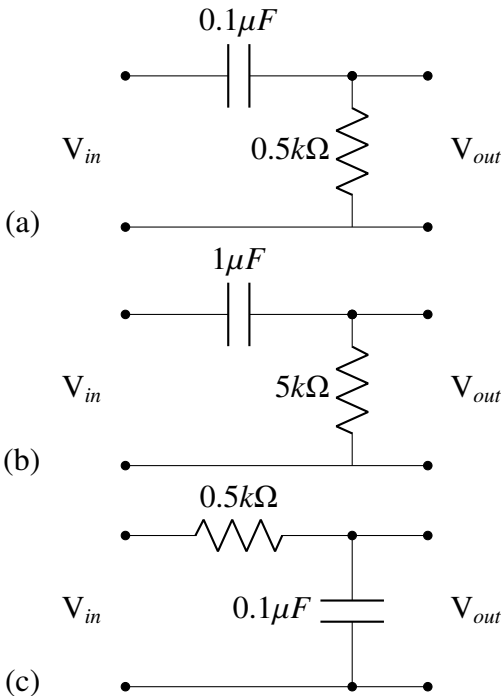

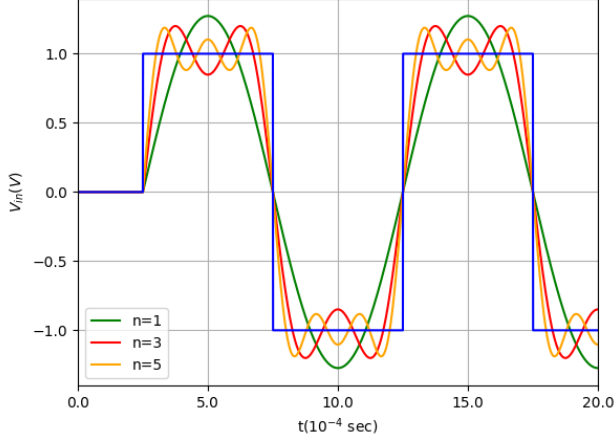


Fig. 2: Input Square Waveform ( $V_{in}(t)$ )

Taking Fourier Transform of  $V_{in}(t)$ :

$$V_{in}(t) \xleftrightarrow{\mathcal{F}} \mathcal{V}_{in}(j\omega) \quad (6)$$

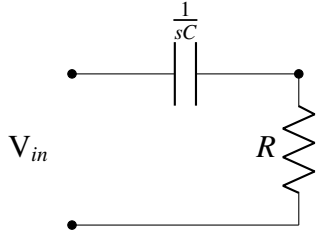


Fig. 3: Series RC Circuit in s-domain

$$s = j\omega \quad (7)$$

$$\Rightarrow Z = R + \frac{1}{sC} \quad (8)$$

$$= R + \frac{1}{j\omega C} \quad (9)$$

$\mathcal{V}_{in}(j\omega)$  was input into all four circuits and Inverse Fourier Transform was taken of the response. Transfer Function:

$$H(j\omega) = \frac{V_{out}}{V_{in}} \quad (10)$$

1) Option A

$$H_R(j\omega) = \frac{R}{R + \frac{1}{j\omega C}} \quad (11)$$

$$= \frac{j\omega RC}{1 + j\omega RC} \quad (12)$$

$$= \left( \frac{\omega RC}{\sqrt{1 + (\omega RC)^2}} \right) e^{j \tan^{-1}(\frac{1}{\omega RC})} \quad (13)$$

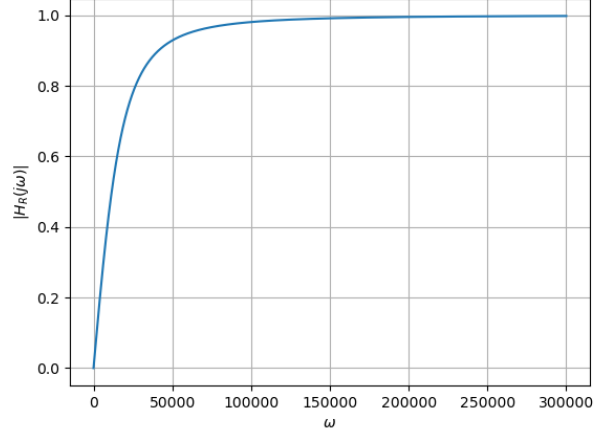


Fig. 4:  $|H_R(j\omega)|$  vs  $\omega$  for  $R = 0.5k\Omega$ ,  $C = 0.1\mu F$

$$\Rightarrow \mathcal{V}_{out}(j\omega) = H_R(j\omega) \mathcal{V}_{in}(j\omega) \quad (14)$$

$$\Rightarrow V_{out}(t) = \mathcal{F}^{-1} \{H_R(j\omega) \mathcal{V}_{in}(j\omega)\} \quad (15)$$

$$(16)$$

Using (5) and (13),

$$V_{out}(t) = \mathcal{F}^{-1} \left( \frac{\omega RC e^{j \tan^{-1}(\frac{1}{\omega RC})}}{\sqrt{1 + (\omega RC)^2}} \right) \sum_{n=1}^{\infty} \frac{4}{n\pi} \sin\left(\frac{n\pi}{2}\right) \cos(n\pi) \cos(n\omega t) \quad (17)$$

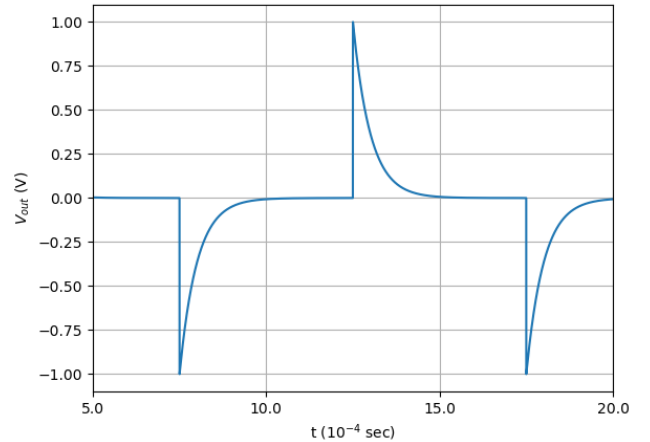



Fig. 5: Opt A:  $V_{out}(t)$  vs  $t$

## 2) Option B

$$H_R(j\omega) = \frac{R}{R + \frac{1}{j\omega C}} \quad (18)$$

$$= \frac{j\omega RC}{1 + j\omega RC} \quad (19)$$

$$= \left( \frac{\omega RC}{\sqrt{1 + (\omega RC)^2}} \right) e^{j \tan^{-1}(\frac{1}{\omega RC})} \quad (20)$$

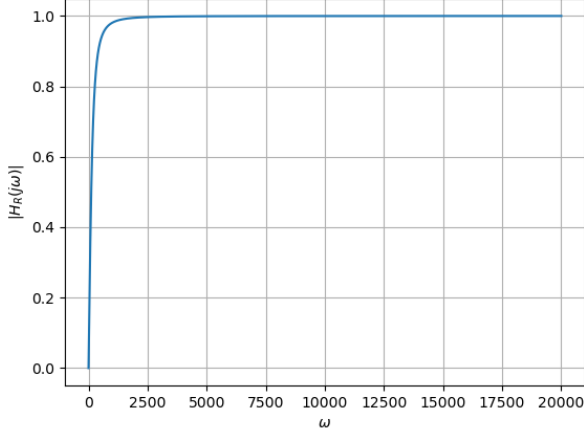
Fig. 6:  $|H_R(j\omega)|$  vs  $\omega$  for  $R = 5k\Omega$ ,  $C = 1\mu F$ 

$$\Rightarrow \mathcal{V}_{out}(j\omega) = H_R(j\omega)\mathcal{V}_{in}(j\omega) \quad (21)$$

$$\Rightarrow V_{out}(t) = \mathcal{F}^{-1} \{H_R(j\omega)\mathcal{V}_{in}(j\omega)\} \quad (22)$$

Using (5) and (20),

$$V_{out}(t) = \mathcal{F}^{-1} \left( \frac{\omega RC e^{j \tan^{-1}(\frac{1}{\omega RC})}}{\sqrt{1 + (\omega RC)^2}} \right) \sum_{n=1}^{\infty} \frac{4}{n\pi} \sin\left(\frac{n\pi}{2}\right) \cos(n\pi) \cos(n\omega t) \quad (23)$$

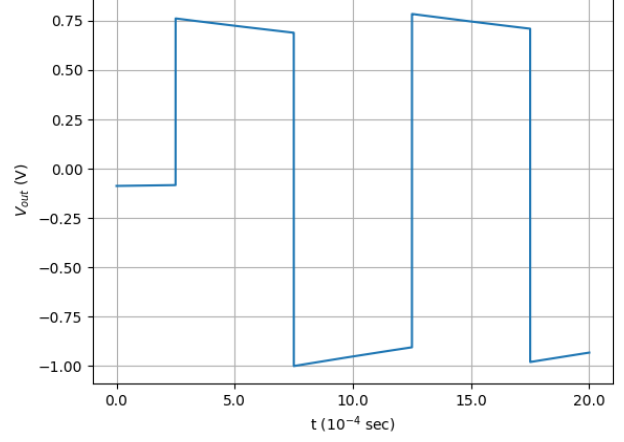
Fig. 7: Opt B:  $V_{out}(t)$  vs  $t$ 

## 3) Option C

$$H_C(j\omega) = \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} \quad (24)$$

$$= \frac{1}{1 + j\omega RC} \quad (25)$$

$$= \left( \frac{1}{\sqrt{1 + (\omega RC)^2}} \right) e^{-j \tan^{-1}(\omega RC)} \quad (26)$$

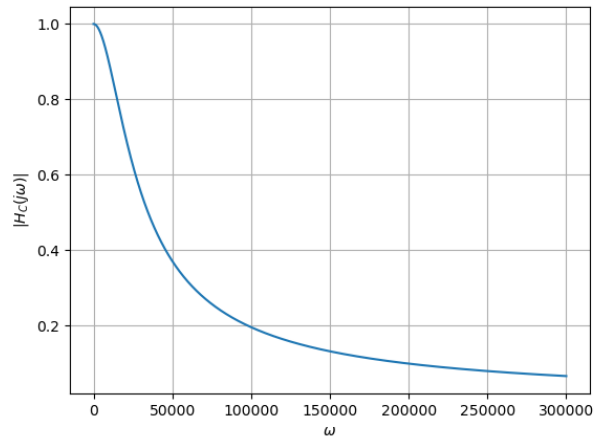Fig. 8:  $|H_C(j\omega)|$  vs  $\omega$  for  $R = 0.5k\Omega$ ,  $C = 0.1\mu F$ 

$$\Rightarrow \mathcal{V}_{out}(j\omega) = H_C(j\omega)\mathcal{V}_{in}(j\omega) \quad (27)$$

$$\Rightarrow V_{out}(t) = \mathcal{F}^{-1} \{H_C(j\omega)\mathcal{V}_{in}(j\omega)\} \quad (28)$$

Using (5) and (26),

$$V_{out}(t) = \mathcal{F}^{-1} \left( \frac{e^{j \tan^{-1}(\frac{1}{\omega RC})}}{\sqrt{1 + (\omega RC)^2}} \right) \sum_{n=1}^{\infty} \frac{4}{n\pi} \sin\left(\frac{n\pi}{2}\right) \cos(n\pi) \cos(n\omega t) \quad (29)$$

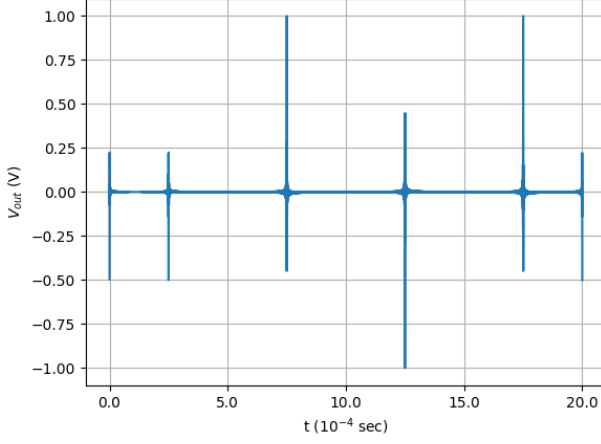


Fig. 9: Opt C:  $V_{out}(t)$  vs  $t$

4) Option D

$$H_C(j\omega) = \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} \quad (30)$$

$$= \frac{1}{1 + j\omega RC} \quad (31)$$

$$= \left( \frac{1}{\sqrt{1 + (\omega RC)^2}} \right) e^{-j \tan^{-1}(\omega RC)} \quad (32)$$

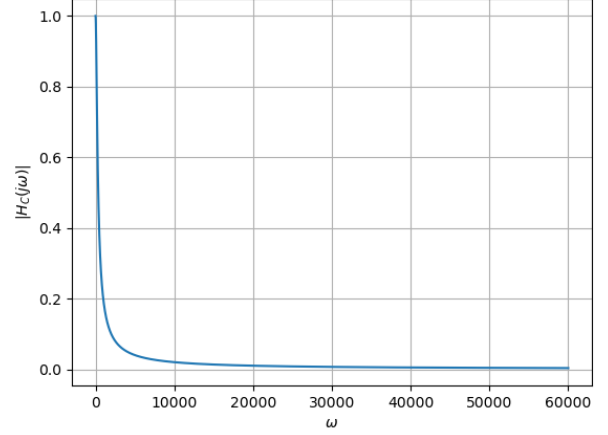


Fig. 10:  $|H_C(j\omega)|$  vs  $\omega$  for  $R = 5k\Omega$ ,  $C = 1\mu F$

$$\Rightarrow \mathcal{V}_{out}(j\omega) = H_C(j\omega) \mathcal{V}_{in}(j\omega) \quad (33)$$

$$\Rightarrow V_{out}(t) = \mathcal{F}^{-1} \{ H_C(j\omega) \mathcal{V}_{in}(j\omega) \} \quad (34)$$

Using (5) and (32),

$$V_{out}(t) = \mathcal{F}^{-1} \left( \frac{e^{j \tan^{-1}(\frac{1}{\omega RC})}}{\sqrt{1 + (\omega RC)^2}} \right) \sum_{n=1}^{\infty} \frac{4}{n\pi} \sin\left(\frac{n\pi}{2}\right) \cos(n\pi) \cos(n\omega t) \quad (35)$$

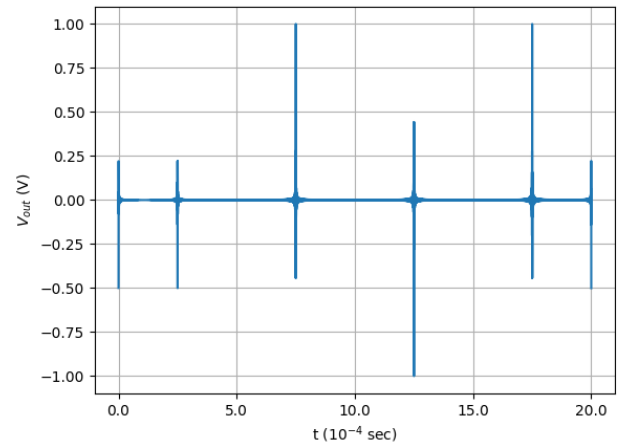


Fig. 11: Opt D:  $V_{out}(t)$  vs  $t$